

## CS220 Assignment-4

### 1) 3 bit gray code Counter

Gray code Counter is a type of counter in which at a time, only one binary digit changes its value.

**Clock** is acting as the input signal according to which states will change.

#### State Assignment

Digit	Gray Code	Assigned State
0	000	S0
1	001	S1
2	011	S2
3	010	S3
4	110	S4
5	111	S5
6	101	S6
7	100	S7

#### State Table

Present State			Next state		
Q2	Q1	Q0	Q2	Q1	Q0
0	0	0	0	0	1
0	0	1	0	1	1
0	1	1	0	1	0
0	1	0	1	1	0
1	1	0	1	1	1

1	1	1	1	0	1
1	0	1	1	0	0
1	0	0	0	0	0

### Excitation and Output Table

Present State			Next State			Flip Flop Excitations			Output
Q2	Q1	Q0	Q2'	Q1'	Q0'	D2	D1	D0	Z
0	0	0	0	0	1	0	0	1	0
0	0	1	0	1	1	0	1	0	0
0	1	1	0	1	0	0	0	1	0
0	1	0	1	1	0	1	0	0	0
1	1	0	1	1	1	0	0	1	0
1	1	1	1	0	1	0	1	0	0
1	0	1	1	0	0	0	0	1	0
1	0	0	0	0	0	1	0	0	1

- K maps

D0

$$D_0 = \overline{s_2} \oplus s_1 \oplus s_0$$

D1

$q_1, q_0$		00	01	11	10
$q_2$	0	0	1	0	0
	1	0	0	1	0

$$D_1 = \overline{q_2} \overline{q_1} q_0 + q_2 q_1 q_0$$

D2

$q_1, q_0$		00	01	11	10
$q_2$	0	0	0	0	1
	1	1	0	0	0


$$D_2 = q_2 \overline{q_1} \overline{q_0} + \overline{q_2} q_1 \overline{q_0}$$


Z(output)

$q_1, q_0$		00	01	11	10
$q_2$	0	0	0	0	0
	1	1	0	0	0

$$Z = q_2 \overline{q_1} \overline{q_0}$$

Circuit Diagram

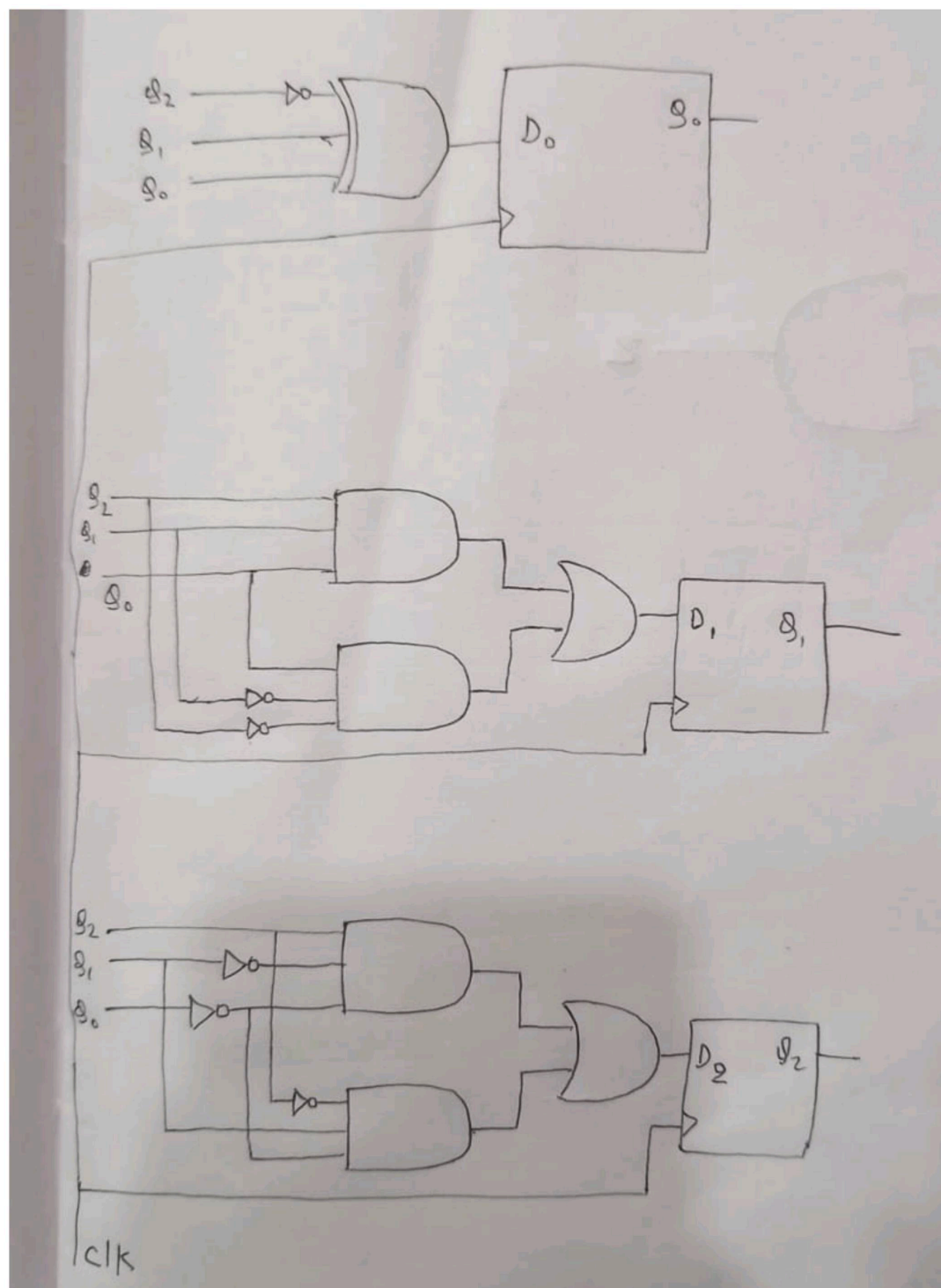

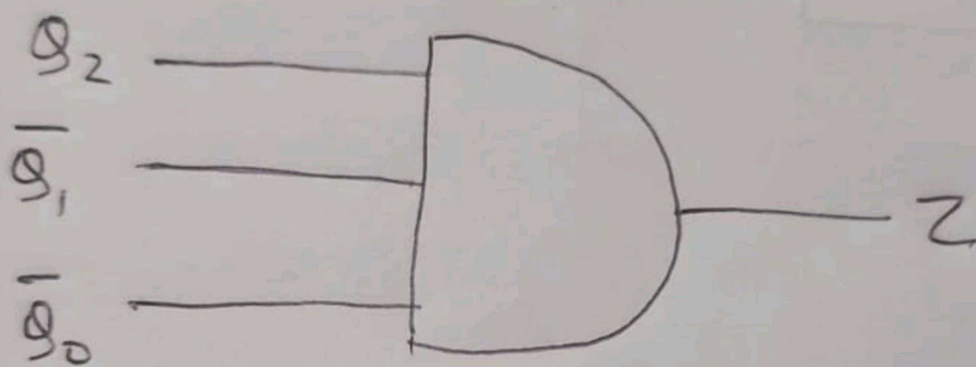

$$Z = q_2 \bar{q}_1 \bar{q}_0$$