

# CS220 Assignment 3

## 1. Sequence Detector (1010):

A sequential detector is a sequential state machine that takes an input string of bits and generates an output 1 whenever the target sequence (1010) is detected. It is implemented by constructing a Finite State Machine (FSM) which allows for overlapping too, i.e, the last bit of one sequence becomes first bit of the next sequence.

We are implementing it through a Mealy machine.

In a Mealy machine, output depends on the present state as well as the external input (X).


FSM construction of Sequence Detector :

- The FSM is implemented using three always blocks, one block for changing the state on getting input ( combinational logic ), one for changing the current state whenever the clock (clk) has positive edge (sequential logic) and one for giving output ( output logic).
- Four states are defined, IDLE, state1, state2, and state3.

```
parameter IDLE = 2'b00, //initially
state1 = 2'b01, //state when it gets 10 from idle state
state2= 2'b10, //state when it gets 101
state3= 2'b11; //state when it gets 1010
```

- Initially, the clock is set 0 and reset is also set 0. Then 8-bit input is given which sends one-bit to the module seq\_detector each time the edge becomes positive in the clock.
- Initially, the state is defined as IDLE and depending upon the input the next state is determined.
- As the state changes, an one-bit output is given. If sequence 1010 gets detected, output is given as 1 else 0.
- Again, when posedge arrives, the next 1-bit input is send, the state changes and the sequence is determined.

❖ State Diagram :

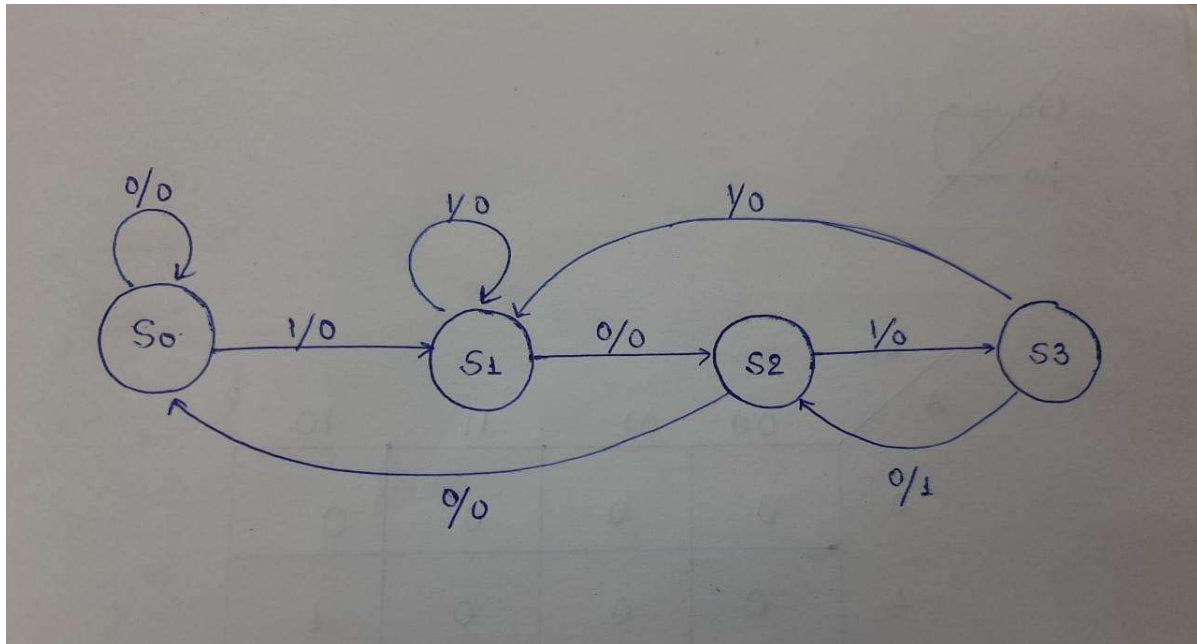

Here S0 is IDLE as stated above.

❖ Output Table :

Present State	Next State		Output	
	X=0	X=1	X=0	X=1
00	00	01	0	0
01	10	01	0	0
10	00	11	0	0
11	10	11	1	0

❖ Excitation Table :

Present State		Input	Next State		Flip-flop excitations		Output
A	B	X	A'	B'	Da	Db	Z
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0
0	1	0	1	0	1	0	0

0	1	1	0	1	0	1	0
1	0	0	0	0	0	0	0
1	0	1	1	1	1	1	0
1	1	0	1	0	1	0	1
1	1	1	1	1	1	1	0

❖ K-map

	$Bx$	00	01	11	10
$A$	0	0	0	0	1
	1	0	1	1	1

$\therefore D_a = Ax + B\bar{x}$



BX		00	01	11	10
A	0	0	1	1	0
	1	0	1	1	0

$D_b = X$

BX		00	01	11	10
A	0	0	0	0	0
	1	0	0	0	1

$Z = AB\overline{X}$

❖ Circuit / Logic Diagram

  

❖ Verilog Code

```
module seq_detector(clk, reset, in, out);
    input clk, reset, in;
    output out;
```

```

wire clk,reset;
wire in; //1-bit input
reg out; //1-bit output
parameter SIZE = 2; //setting parameter SIZE as 2

//setting parameters as different states
parameter IDLE = 2'b00, //initially
state1 = 2'b01, //state when it gets 10 from idle state
state2= 2'b10, //state when it gets 101
state3= 2'b11; //state when it gets 1010

reg [SIZE-1:0] state; //current state
reg [SIZE-1:0] next_state; //next state
initial begin
    state = IDLE;
end

always @(state or in) begin
    next_state= IDLE;
    case (state)

        //when it gets input after it is at IDLE state
        IDLE: if (~in) begin

            next_state= IDLE;
        end
        else begin
            next_state = state1;
        end

        //when it gets input after it is at state1
        state1: if(~in) begin

            next_state = state2;
        end
        else begin
            next_state= state1;
        end
    endcase
end

```

```

        end

        //when it gets input after it is at state2
        state2: if(~in) begin

            next_state = IDLE;
        end
        else begin
            next_state = state3;
        end

        //when it gets input after it is at state3
        state3: if(~in) begin
            next_state= state2;
        end
        else begin
            next_state = state1;
        end

        default: begin
            next_state = IDLE;
        end

    endcase

end

always @(posedge clk) begin

    if(reset == 1'b1) begin

        state = IDLE; //new (8-bit) input
    end
    else begin

        state = next_state; //continuation of the input
    end

end

```

```

always @(state or in) begin

    if(reset == 1'b1) begin
        out = 1'b0;
    end

    else begin
        if(state == state3) begin
            if(in == 1'b0) begin
                out = 1'b1; //output when it finds the sequence of
1010
            end
            else begin
                out = 1'b0; /////output when it is at any other state
            end
        end
        else begin
            out = 1'b0;
        end
    end

end

endmodule

```

★ Testbench :

```

`include "A3_Q1_seq_detector.v"

module seq_tb();

reg clk, reset, inp;
reg [7:0] in; //reg to store 7-bit input
reg [7:0] out; //reg to store 7-bit output
wire outp; //to store 1-bit after each 1-bit input

```



```

integer i;

always #2 clk=~clk; //oscillation in clock

seq_detector x(clk,reset,inp,outp);

initial begin
    clk= 1'b0; //setting clock to 0 initially
    reset = 1'b0; //setting reset to 0 initially and after each input
case changing to 1 to get again IDLE state
    in = 8'b10101010; #35 $display("input = %b output= %b",in,out);
    reset = 1'b1;
    #5 reset =1'b0;
    in = 8'b01110110; #35 $display("input = %b output= %b",in,out);
    reset = 1'b1;
    #5 reset =1'b0;
    in = 8'b01010010; #35 $display("input = %b output= %b",in,out);
    reset = 1'b1;
    #5 reset =1'b0;
    in = 8'b10100010; #35 $display("input = %b output= %b",in,out);
    reset = 1'b1;
    #5 reset =1'b0;
    in = 8'b01011010; #35 $display("input = %b output= %b",in,out);
    reset = 1'b1;
    #5 reset =1'b0;
    in = 8'b01010110; #35 $display("input = %b output= %b",in,out);
    reset = 1'b1;
    #5 reset =1'b0;
    in = 8'b00010010; #35 $display("input = %b output= %b",in,out);
    reset = 1'b1;
    #5 reset =1'b0;
    in = 8'b00010110; #35 $display("input = %b output= %b",in,out);
    reset = 1'b1;
    #5 reset =1'b0;
    in = 8'b11001010; #35 $display("input = %b output= %b",in,out);
    reset = 1'b1;
    #5 reset =1'b0;
    in = 8'b01110011; #35 $display("input = %b output= %b",in,out);
    reset = 1'b1;

```

```

#5 reset =1'b0;
in = 8'b01110100; #35 $display("input = %b output= %b",in,out);
reset = 1'b1;
#5 reset =1'b0;
in = 8'b11010010; #35 $display("input = %b output= %b",in,out);
reset = 1'b1;
#5 reset =1'b0;
in = 8'b01010110; #35 $display("input = %b output= %b",in,out);
reset = 1'b1;
#5 reset =1'b0;
in = 8'b00010010; #35 $display("input = %b output= %b",in,out);
reset = 1'b1;
#5 reset =1'b0;
in = 8'b01010000; #35 $display("input = %b output= %b",in,out);

#5 $finish;

end

//giving input bit-wise whenever the 7-bit input changes
always @(in) begin
    for(i=7;i>=0;i--1) begin
        #2
        inp= in[i];
        #2
        out[i]= outp;
    end
end

endmodule

```