

3-bit odd parity bit generator:

A 3-bit odd parity bit generator takes 3 bits input one by one and generates an output 1 if the number of 1s are even or 0 otherwise. It can be implemented by Finite State Machine (FSM) which keeps count as states. It is a type of Moore Machine which gives output on the basis of Current State .

FSM Construction of 3-bit odd parity generator :

- The FSM is implemented using three always blocks, one block for changing the state on getting input (combinational logic), one for changing the current state whenever the clock (clk) has positive edge (sequential logic) and one for giving output (output logic).
- 11 states are defined, IDLE, odd0_even0, odd0_even1, odd1_even0, odd0_even2, odd1_even1, odd2_even0, odd2_even1, odd1_even2, odd3_even0, odd3_even1

- We are defining the states on the basis of number of 0 and 1 we encounter, for eg odd2_even1 means 2 bits are 1(odd) and 1 bit is 0(even)

- .

States :

```

• IDLE = 4'b0000,
• odd0_even0 = 4'b1000,
• odd0_even1 = 4'b0010,
• odd1_even0 = 4'b0001,
• odd0_even2 = 4'b0110,
• odd1_even1 = 4'b0011,
• odd2_even0 = 4'b0101,
• odd0_even3 = 4'b1110,
• odd1_even2 = 4'b0111,
• odd2_even1 = 4'b1011,
• odd3_even0 = 4'b1101;

```

- Initially, the clock is set 0 and reset is also set 0. Then 3-bit input is given which sends one-bit to the module parity_gen each time the edge becomes positive in the clock.
- Initially, the state is defined as IDLE and depending upon the input the next state is determined.
- The input changes each time the edge becomes positive in the clock and at the end of the 3-bit input, output is given as 1 in case the number of 1's in the sequence is even, 0 in other case.

Truth Table:-

| Inputs (3-bits) | | | Output |
|-----------------|---|---|--------|
| A | B | C | O |
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |


| | | | |
|---|---|---|---|
| 1 | 1 | 1 | 0 |
|---|---|---|---|

K-Map

| | | BC | | | |
|---|---|----|----|----|----|
| | | 00 | 01 | 11 | 10 |
| A | 0 | 1 | 0 | 1 | 0 |
| | 1 | 0 | 1 | 0 | 1 |

$$\begin{aligned}\text{Output} &= A'B'C' + AB'C + A'BC + ABC' \\ &= A \oplus (B \oplus C)'\end{aligned}$$

Logic Circuit:

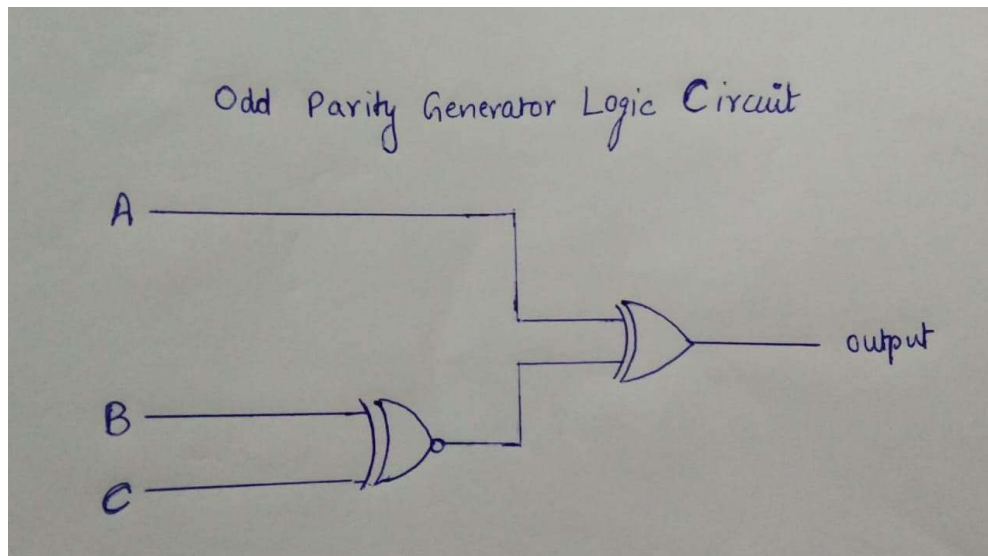


Excitation Table:

For any input with new (8-bit)input the state changes to IDLE_ state

| Previous State | Next State | Input | Output |
|----------------|------------|-------|--------|
| 0000 | 1000 | 0/1 | 0 |
| 1000 | 0001 | 1 | 0 |
| 1000 | 0010 | 0 | 0 |

| | | | |
|------|------|-----|---|
| 0010 | 0110 | 0 | 0 |
| 0010 | 0011 | 1 | 0 |
| 0001 | 0011 | 0 | 0 |
| 0001 | 0101 | 1 | 0 |
| 0110 | 1110 | 0 | 0 |
| 0110 | 0111 | 1 | 0 |
| 0011 | 0111 | 0 | 0 |
| 0011 | 1011 | 1 | 0 |
| 0101 | 1011 | 0 | 0 |
| 0101 | 1101 | 1 | 0 |
| 1110 | 0000 | 0/1 | 1 |
| 0111 | 0000 | 0/1 | 0 |
| 1011 | 0000 | 0/1 | 1 |
| 1101 | 0000 | 0/1 | 0 |

State diagram:

 

Moore state diagram of 3 bit parity generator

Verilog code:

```

module parity_gen(clk,reset,in,out);

input clk,reset,in;
output out;

wire clk,reset;
wire in; //1-bit input
reg out; //1-bit output
parameter SIZE = 4; //setting parameter SIZE as 4

//setting parameters as different states
parameter IDLE = 4'b0000, //initial state
odd0_even0 = 4'b1000, //state when there are zero 1s and zero 0s
odd0_even1 = 4'b0010, //state when there are zero 1s and one 0s
odd1_even0 = 4'b0001, //state when there are one 1s and zero 0s
odd0_even2 = 4'b0110, //state when there are zero 1s and two 0s
  
```

```
odd1_even1 = 4'b0011, //state when there are one 1s and one 0s
odd2_even0 = 4'b0101, //state when there are two 1s and zero 0s
odd0_even3 = 4'b1110, //state when there are zero 1s and three 0s
odd1_even2 = 4'b0111, //state when there are one 1s and two 0s
odd2_even1 = 4'b1011, //state when there are two 1s and one 0s
odd3_even0 = 4'b1101; //state when there are three 1s and zero 0s
```

```
reg [SIZE-1:0] state; //current state
reg [SIZE-1:0] next_state; //next state
initial begin
    state = IDLE;
end
```

```
always @(state or in) begin
```

```
    next_state= IDLE;
    case (state)
        IDLE: next_state= odd0_even0;
```

```
        //when it gets input after it is at odd0_even0 state
```

```
        odd0_even0 :if (in) begin
            next_state= odd1_even0;
```

```
        end
```

```
        else begin
```

```
            next_state= odd0_even1;
```

```
        end
```

```
        //when it gets input after it is at odd0_even1 state
```

```
        odd0_even1 : if (in) begin
            next_state= odd1_even1;
```

```
        end
```

```
        else begin
```

```
            next_state= odd0_even2;
```

```
        end
```

```
        //when it gets input after it is at odd1_even0 state
```

```
        odd1_even0: if(in) begin
            next_state= odd2_even0;
```

```
        end
```

```
else begin
    next_state= odd1_even1;
end

//when it gets input after it is at odd0_even2 state
odd0_even2: if(in) begin
    next_state= odd1_even2;
end
else begin
    next_state= odd0_even3;
end

//when it gets input after it is at odd1_even1 state
odd1_even1: if(in) begin
    next_state= odd2_even1;
end
else begin
    next_state= odd1_even2;
end

//when it gets input after it is at odd2_even0 state
odd2_even0: if(in) begin
    next_state= odd3_even0;
end
else begin
    next_state= odd2_even1;
end

//when it gets input after it is at odd0_even3 state
odd0_even3: if(in) begin
    next_state= IDLE;
end
else begin
    next_state= IDLE;
end

//when it gets input after it is at odd1_even2 state
odd1_even2: if(in) begin
    next_state= IDLE;
end
```

```

        else begin
            next_state= IDLE;
        end

        //when it gets input after it is at odd2_even1 state
        odd2_even1: if(in) begin
            next_state= IDLE;
        end
        else begin
            next_state= IDLE;
        end

        //when it gets input after it is at odd3_even0 state
        odd3_even0: if(in) begin
            next_state= IDLE;
        end
        else begin
            next_state= IDLE;
        end
        default: next_state = IDLE;
    endcase
end

always @(posedge clk ) begin
    if(reset) begin
        state = #1 IDLE; //new (3-bit) input
    end
    else begin
        state = #1 next_state; //continuation of the input
    end
end

always @(in or state ) begin
    //output when it is at state with odd number of ones
    if(state == odd2_even1) begin
        out = #1 1'b1;
    end
    else if(state == odd0_even3) begin
        out = #1 1'b1;
    end
end

```



```

        end
        else begin
            out = #1 1'b0; //otherwise condition
        end
    end

end

endmodule

```

Testbench:

```

`include "A3_Q2_parity_gen.v"

module tstbnch();

    reg clk,reset,inp,out;
    reg [2:0] in; //input register
    wire outp; //output wire
    integer i;

    always #1 clk = ~clk; //for clock oscillation

    parity_gen x(clk,reset,inp,outp);

    initial begin
        clk = 1'b0; //setting clock to 0 initially
        reset = 1'b0; //setting reset to 0 initially and after each input case
        changing to 1 to get again IDLE state
        in = 3'b000;
        #10
        $display("input=%b parity_bit=%b",in,outp);
        reset=1'b1;
        #5 reset=1'b0;
        in = 3'b001;
        #10
        $display("input=%b parity_bit=%b",in,outp);
        reset=1'b1;
    end
endmodule

```

```
#5 reset=1'b0;
in = 3'b010;
#10
$display("input=%b parity_bit=%b",in, outp);
reset=1'b1;
#5 reset=1'b0;
in = 3'b011;
#10
$display("input=%b parity_bit=%b",in, outp);
reset=1'b1;
#5 reset=1'b0;
in = 3'b100;
#10
$display("input=%b parity_bit=%b",in, outp);
reset=1'b1;
#5 reset=1'b0;
in = 3'b101;
#10
$display("input=%b parity_bit=%b",in, outp);
reset=1'b1;
#5 reset=1'b0;
in = 3'b110;
#10
$display("input=%b parity_bit=%b",in, outp);
reset=1'b1;
#5 reset=1'b0;
in = 3'b111;
#10
$display("input=%b parity_bit=%b",in, outp);
```

```
#3$finish;
```

```
end
```

```
//giving input bit-wise whenever the 3-bit input changes

always @(in) begin

    for(i=0;i<3;i+=1) begin
        #2
        inp= in[i];

    end

end

end

always @(outp) begin
    // $display("outpchange %d",$time);

end

endmodule
```