

Johnson Counter

Johnson counter is like a ring counter with an advantage that a n bit johnson counter can have $2*n$ different states but a normal one has only n .

It is made up of n flip flops where the output of one flip flop acts as the input of next one and the input of first one is negation of the output of the last one.

The output of each flip flop makes up the total state of the counter.

Working

Initially clear is set to 1 and 8 bit output is set to 0.


Then clear is set to 0 so that we can start with the functioning of the counter. So the first flip flop get the input 1 (as output of last one is still 0).

As we are using D flip flop it will give output the same as input till the next rising edge of the clk. So we will get 10000000 as output.

Then in 2nd clock rise, we will get the 2nd flipflop's input also to be high so the output now will be 11000000

In similar fashion, after each rising edge of the clk, we will get different states depending on the previous state.

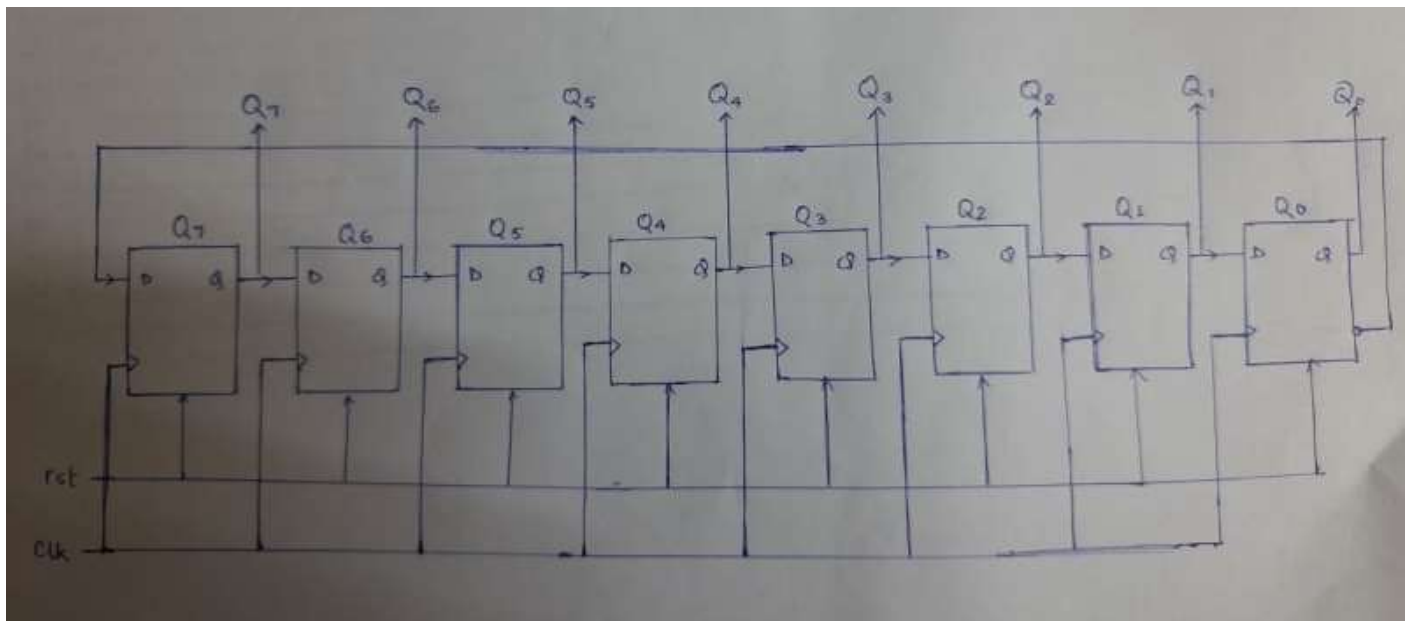If we give the reset as 1, it will reset all the flip flop output to 0.



Circuit diagram

After keeping reset 0, this will be the truth table of this counter

Clock pulse	Q7	Q6	Q5	Q4	Q3	Q2	Q1	Q0
0	0	0	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0
2	1	1	0	0	0	0	0	0
3	1	1	1	0	0	0	0	0
4	1	1	1	1	0	0	0	0
5	1	1	1	1	1	0	0	0
6	1	1	1	1	1	1	0	0
7	1	1	1	1	1	1	1	0
8	1	1	1	1	1	1	1	1
9	0	1	1	1	1	1	1	1
10	0	0	1	1	1	1	1	1
11	0	0	0	1	1	1	1	1
12	0	0	0	0	1	1	1	1
13	0	0	0	0	0	1	1	1
14	0	0	0	0	0	0	1	1
15	0	0	0	0	0	0	0	1

From the truth table, we can see that at first, high flip flops increase from the left, then all the bits are high, after that they decrease towards the right .

Some of the drawbacks of it are:

- It does not give output in the serialized manner.
- Still many if the states are not being used.